$\mathcal{N}CTU$ -EE $\mathcal{D}CS - 2017$

Lab01 Exercise

Design: BCD

Data Preparation

1. Extract test data from TA's directory:

% tar -xvf ~dcsta02/ Lab01.tar

- 2. The extracted LAB director contains:
 - a. 01_RTL/ : your exercise

Design Description

This exercise is a design for Binary-Coded Decimal(BCD).

There are 3 outputs in this design, each represents hundreds, tens, and units digit.

Inputs

1. There is only 1 input, and the value is from 0 to 511.


Outputs

- 1. Three outputs **out_hundred** [2:0], **out_ten**[3:0], and **out_unit**[3:0] represent hundreds, tens, and units digit of input signal.
- 2. When **input** signal is given, outputs should change at the same cycle.

Specifications

- 1. Top module name : **BCD**(File name : **BCD.v**)
- 2. Input pins: **in_bin** [8:0].
- 3. Output pins: out_hundred [2:0], out_ten [3:0], out_unit [3:0].

Block Diagram

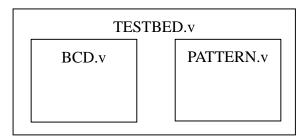

Note

1. Grading policy:

In this bonus lab, pattern are already given. You have to make sure you pass the

pattern before demo, TAs will test your design with the given pattern again during demo.

Design: 100%

2. Template folders and reference commands:

01_RTL/ (RTL simulation) → ./01_run

02_SYN/ (RTL synthesis) → ./01_run_dc

3. Sample Waveform:

